


ANALYSE ET RÉOLUTION DE CIRCUITS LINÉAIRES

MÉTHODES D'ANALYSE ET DE RÉOLUTION – SOURCES DE TENSION ET SOURCES DE COURANT

LEÇON 7

Électrotechnique I

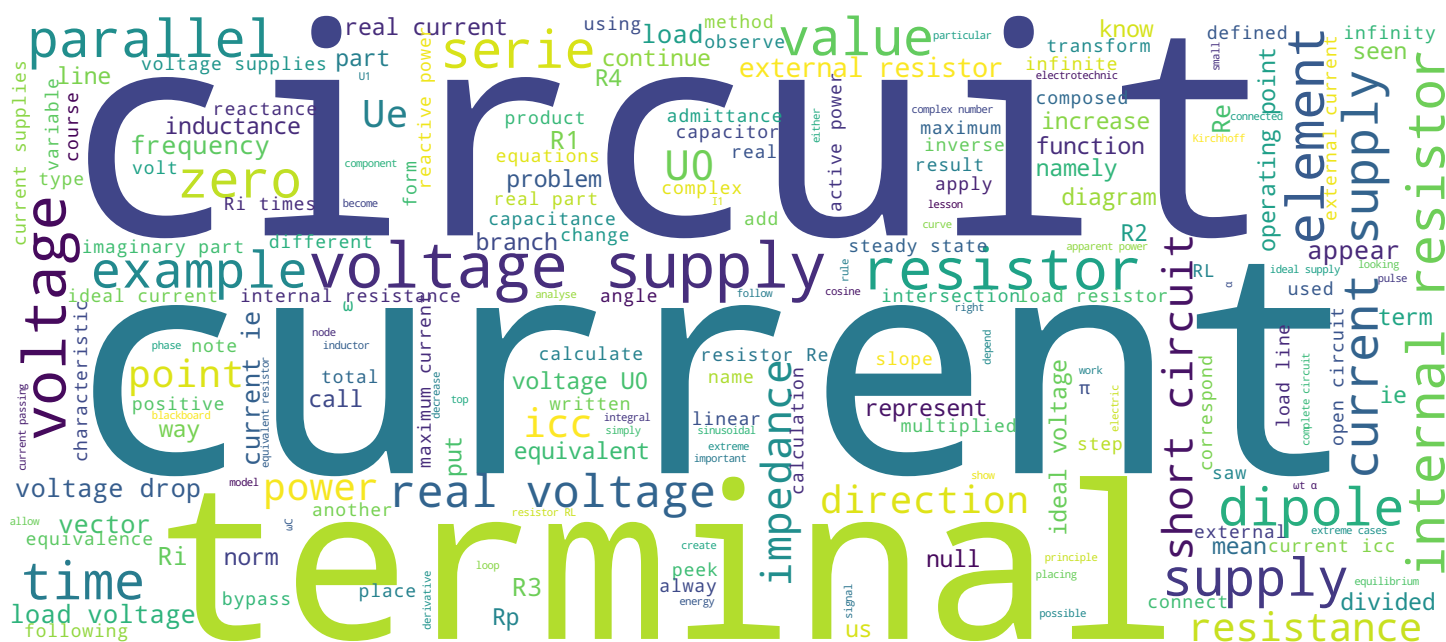Yves PERRIARD & Paolo GERMANO
Laboratoire d'Actionneurs Intégrés



Video



Généralités



- Méthode d'analyse et de résolution
 - Étapes
- Source de tension réelle
- Source de courant réelle
- Equivalence

Electrotechnique I

Hello. In this course up to now, we have seen the three linear elements that are the resistance, the inductance and the capacitance, as well as voltage supplies, ideal current supplies. We have also seen various methods to combine these elements, in series, in parallel, and we saw a few simple circuits. In today's lesson, we will see resolution methods for a complete circuit. Today we will initially see the methods to analyse a circuit, which is a sequel of a series of steps that let us arrive to the desired result. In a second part, we will see real voltage and current supplies and finally, we will see the equivalence between these two supply types.

Notes


Summary



0m 04s

Étapes

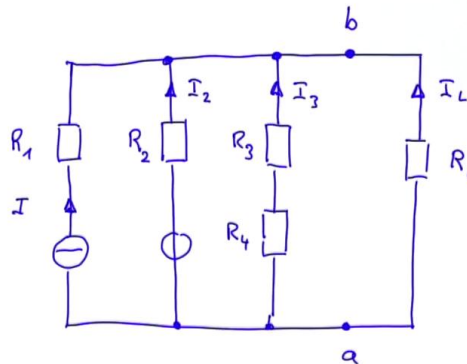1. Représenter le schéma
2. Définir toutes les grandeurs
3. Définir le sens des tensions et des courants
4. Réduire le schéma
5. Analyser le circuit



Electrotechnique I

So, the different steps to resolve a circuit are, firstly, to schematically represent the circuit, whether it is given, or transcribed from a wording. We then represent here and example of a diagram with resistances, and voltage supplies. [Silence] So, we represent all the circuit's elements: resistors, current supplies, voltage supplies, and eventually other contact points. We also give a name to these points, for example the circuit's terminals b and a, and once all the elements are represented, we give them a name: the resistor R1, the resistor R2, the resistor R3 and R4, and here, for example, a resistor RL, which is a load resistor. We now define the currents and voltages: current I, for example, here, and then in each branch, we will also give a name to the current that is going through it: I2, I3, and in the last branch, current IL. In principle, before resolving the problem, we do not know in which direction the current, here: the currents I3, I2 and IL, will go through the circuit's branch. So in principle, we choose a direction for the current. If the current is chosen a priori, I would say, as going the wrong way, well we will get a negative numerical value. That is not a problem.

Notes


Summary



0m 57s

Étapes

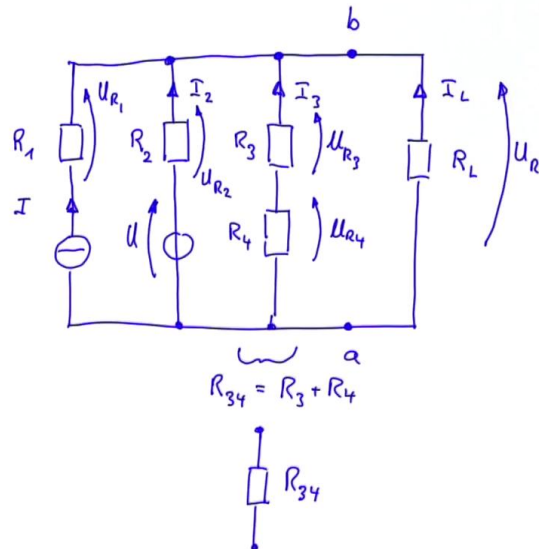1. Représenter le schéma
2. Définir toutes les grandeurs
3. Définir le sens des tensions et des courants
4. Réduire le schéma
5. Analyser le circuit



Electrotechnique I

However, what is important, is to define in a coherent way the voltage drops at the terminals of each elements, for example here, on the resistance R_3 , we will have a voltage drop in the same direction as the current I_3 , so, we are obligated to define here a tension that we will call U_{R3} in the positive direction like this. Likewise for the voltage U_{R4} . The voltage U_{R2} is defined as positive in the direction of the current, and the voltage U_{R1} is also positive in the current's direction. The last voltage, it is the voltage at the terminals of the load, which is going from bottom to top, from terminal a towards terminal b. We are still missing what the wording has given us: the voltage supply U , which imposes a voltage in that direction. So, that is a given problem. Once all the values have been defined with a given direction, we can start reducing the diagram. For example here, we see that we can put the two resistors R_4 and R_3 in series with an equivalent resistors that we can call R_{34} , which is equal to $R_3 + R_4$, and that would replace the two resistors R_3 and R_4 . As a reminder, two resistors or two element are in series when the same current is going through them, [Writes on the blackboard] and two elements are in parallel when they are connected on the same terminals.

Notes


Summary



3m 22s

Étapes

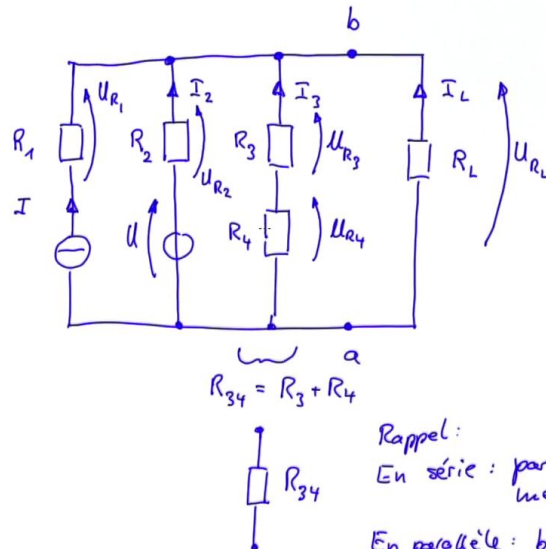1. Représenter le schéma
2. Définir toutes les grandeurs
3. Définir le sens des tensions et des courants
4. Réduire le schéma
5. Analyser le circuit



Electrotechnique I

[Writes on the blackboard] We can see in our example that R3 and R4 are in series since the same current is going through them, and for example, R2 is not in parallel with R1 because this terminal is the same, but this one isn't. On the other hand, the equivalent resistor R34 is in parallel with the resistor RL since they share the same terminals. We talked today about two types of simplifications: in series or in parallel, thereafter we will see other simplification methods.


Notes

Summary



5m 37s

Schéma - Définition des grandeurs

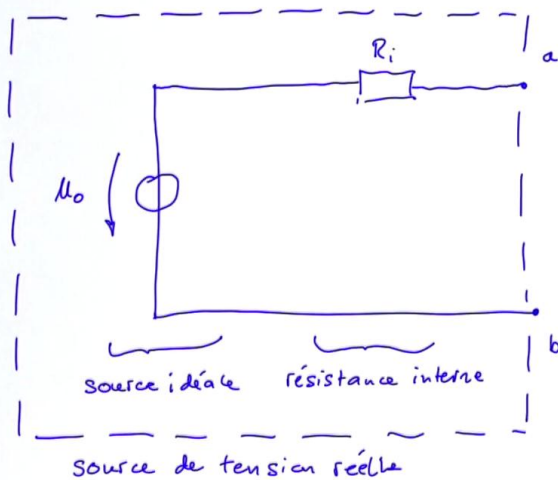

Electrotechnique I

We will now analyse the case of a real voltage supply. It is composed of an ideal voltage supply, like this, with a value U_0 , but an ideal voltage supply never exists alone. Why? Because we see that if we bypass these voltage supplies, there will be an infinite current in this bypass and so the power provided by the supply would be of U_0 times infinity, which has no more physical sense, and moreover, we know that there is a zero voltage at the terminals of a short circuit, we bypass a voltage U_0 , and a zero voltage, that makes no sense, neither mathematical, nor physical. So this real voltage supply is always combined with a resistance that we call here internal resistor. This internal resistor, we place it in series with the voltage supply. Placing it in parallel would again make no sense because if we bypass the voltage supply, and then the resistor in parallel, we have the same problematic of infinite power, so we place an internal resistor in series. So this is the ideal supply, this is the internal resistance in series, and the whole makes a real voltage supply. We can define two terminals to this real voltage supply, boundary a and boundary b. The voltage supply will also be used to supply a load.


Notes

Summary



6m 28s

Schéma - Définition des grandeurs

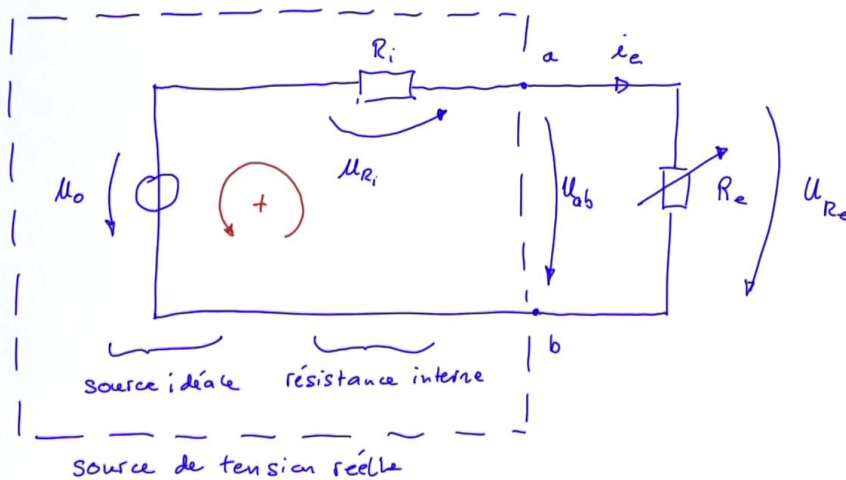

Electrotechnique I

We will place here a load resistor that we will call R_e , the subscript e being used for external, which means that it is an element that is external to the supply, this resistor can be variable, it can go from zero to infinity, and we show with this arrow here that it is variable. To follow on, there will be a current that settles in the circuit and that we will call i_e . We can now define all the voltages at the terminals of our circuit. We have the supply voltage U_0 , we have a voltage drop here, on the internal resistor that we call U_{R_i} , a voltage that appears at the terminals of the dipole U_{ab} which is equal to the voltage drop, the voltage that appears on the boundaries of the external resistor U_{R_e} . Let's define a positive direction for the voltage in this loop. We will now characterise this dipole, this real voltage supply.

Notes

Summary



8m 41s

Mise en équation - Caractérisation


Par Kirchhoff : $\sum u = 0$

$$u_0 - u_{R_i} = u_e$$

$$u_0 - R_i \cdot i_e = R_e \cdot i_e$$

$$u_0 = i_e (R_e + R_i)$$
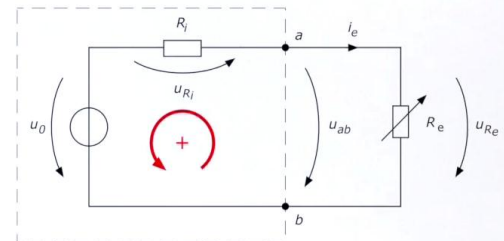
$$i_e = \frac{u_0}{R_e + R_i} \quad \text{et} \quad u_e = u_0 \cdot \frac{R_e}{R_e + R_i}$$



Electrotechnique I

By Kirchhoff, we can write that: the sum of voltages in a loop is equal to zero. We apply this to our circuit and we see that the real voltage supply minus the voltage drop on our internal resistor is equal to the external voltage of the circuit or the dipole. By developing these terms U_{R_i} and U_e we get that the voltage supply minus R_i times the current going through it is equal to the external resistor times the current. By developing this equation, we get that the voltage is equal to i_e , which multiplies R_e plus R_i , and this lets us determine the operating point of the circuit, meaning that the current i_e , the current passing through the circuit, is equal to the no-load voltage, or the voltage of the ideal supply, divided by R_e plus R_i . More still, the voltage at the terminals of the dipole U_e , is equal to U_0 , the ideal voltage supply, multiplied by R_e over $R_e + R_i$. This equation is simply R_e times the current i_e . i_e and U_e give us the operating point. Lets look for the operating limits of this supply, namely, the extreme cases when the internal resistor is infinite, which is the case when we have an open circuit.

Notes

Summary



Mise en équation - Caractérisation

Par Kirchhoff : $\sum u = 0$

$$u_0 - u_{R_i} = u_e$$

$$u_0 - R_i \cdot i_e = R_e \cdot i_e$$

$$u_0 = i_e (R_e + R_i)$$

$$i_e = \frac{u_0}{R_e + R_i} \quad \text{et} \quad u_e = u_0 \cdot \frac{R_e}{R_e + R_i}$$

- Si $R_e = \infty$ (circuit ouvert) $\rightarrow u_e = u_0$ "à vide" ($i_e = 0$)
- Si $R_e = 0$ (circuit fermé) $\rightarrow u_e = 0$ "en court-circuit" $i_e = i_{cc} = \frac{u_0}{R_i}$

Electrotechnique I

So if R_e is equal to infinity, open circuit, well the voltage U_e that appears at the supply's terminals is equal to U_0 , there is no current in the circuit, so there is no voltage drop at the terminals of the resistance R_i and so we find the voltage U_0 at the terminals of the dipole, we take about no-load operation, the external current is equal to zero. Another extreme case, this time if the internal resistor is equal to zero, we take of a closed circuit, well U_e , since the terminals are short-circuited, is equal to zero. We are in a short-circuit state in which the external current is equal to the short-circuit current, which is the maximum current that can be provided by the supply, and that is equal to U_0 over R_i . If we observe these equations in a plane or in a current-voltage diagram, we get the following thing: on the abscissa, we have the current circulating through the circuit, on the ordinate, we have the voltage that appears at the terminals of the dipole U_e , at if we take the extreme points, when the external resistor is equal to zero; we are in an open circuit, we have a voltage that appears of value U_0 , which is the no-load operation.

Notes

Summary



Mise en équation - Caractérisation

Par Kirchhoff : $\sum u = 0$

$$u_0 - u_{R_i} = u_e$$


$$u_0 - R_i \cdot i_e = R_e \cdot i_e$$

$$u_0 = i_e (R_e + R_i)$$

$$i_e = \frac{u_0}{R_e + R_i} \quad \text{et} \quad u_e = u_0 \cdot \frac{R_e}{R_e + R_i}$$

- Si $R_e = \infty$ (circuit ouvert) $\rightarrow u_e = u_0$ "à vide" ($i_e = 0$)
- Si $R_e = 0$ (circuit fermé) $\rightarrow u_e = 0$ "en court-circuit" $i_e = i_{cc} = \frac{u_0}{R_i}$

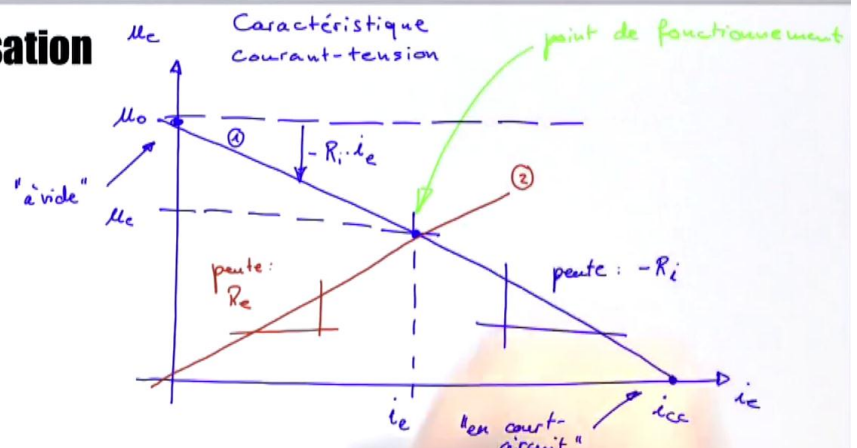① Caractéristique U-I ② Droite de charge.



Electrotechnique I


The other extreme case, when the resistor is zero, we have this point here, the resistor is null so the voltage at the terminals of the circuit is null and we have here a maximum current, which is the current i_{cc} , it is the short-circuit operating mode. All the elements of the circuit being linear, we can trace a line between these two points, which will give us the characteristics of the circuit. The operating point will be on this line, corresponding to a value of i_e , and a voltage at the terminals of the circuit that is equal to u_e . This intersection is the result of the intersection of two lines, the supply characteristic is a line corresponding to the external resistor. This first line corresponds to this equation and the second line to this equation. We see that the blue curve corresponds to a no-load voltage from which we subtract R_i times i_e , so the slope is equal to minus R_i . The slope of the second line is equal to R_e . The curve 1 is called characteristic of U_i and the curve 2 is called load line.

Notes

Summary



Mise en équation - Caractérisation

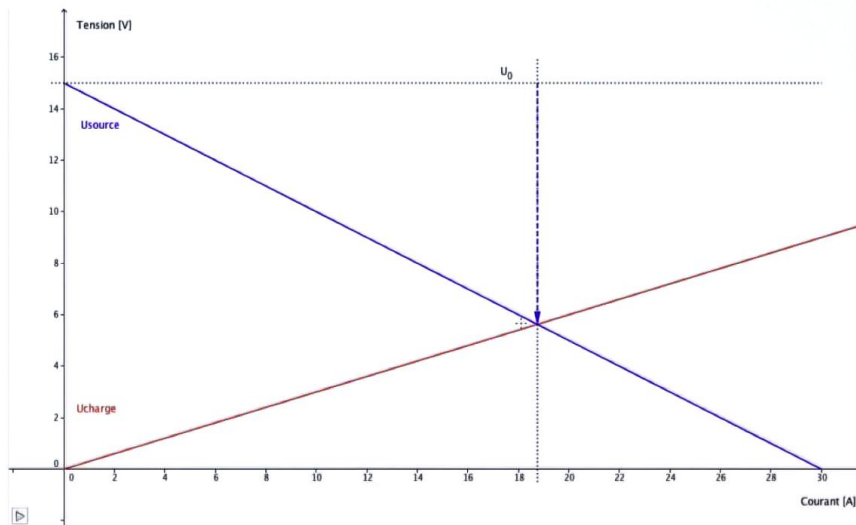


Electrotechnique I

If we observe here the current-voltage characteristic of a given real voltage supply, we see that it is characterised by a no-load voltage U_0 , here of 15 volts, and a slope, having a characteristic whose slope is given by the internal resistor R_i , of a given value. If we improve this supply and we diminish the internal resistor, we get a smaller slope, a smaller internal resistor. If we continue to improve this internal resistor, we see that the characteristic slope of U_i continues to decrease, we remark that the maximal current provided by the supply is increasing. If we represent, for this last voltage supply, the load line that corresponds to the external resistor that we apply to the dipole, we see that the operating point is given by the intersection of the characteristic U_i and the load line, the operating point is here, we observe the output voltage of the dipole and the current passing through this dipole. If we change the load, and so the circuit's resistance, in this example we increase the load, and so we diminish the resistance, we see that the voltage at the terminals of the dipole falls and that the current increases. If we continue to increase the load, so we continue to decrease the resistance, well the voltage at the terminals of the dipole will continue to fall and the current will continue to increase. We note here the voltage drop on the internal resistor.

Notes

Summary



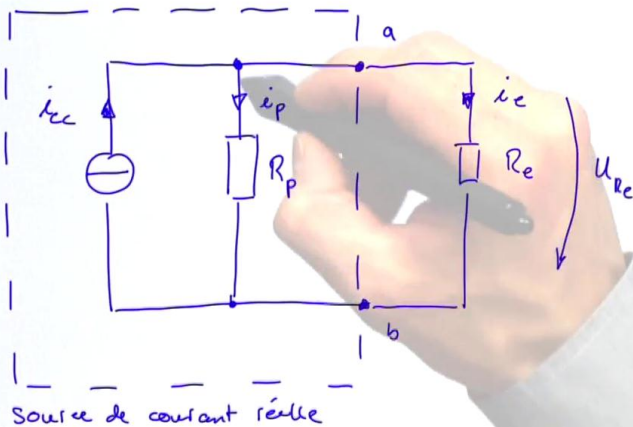


Electrotechnique I

Lets now look at the case of a real current supply. So the real current supply is composed of an ideal current supply in parallel, this time, with an internal resistor, that we call R_p . The value of this current supply is i_{cc} . This constitutes a dipole that has two poles a and b , and that we call real current supply. We note this time that the resistor is in parallel; why? Because if we had put it in series, the current supply imposing a current i_{cc} , well, in the case of a short-circuit, for example, on the supply, would lead to a physical impossibility of having an infinite power, so we put this resistor R_p in parallel. We can do the same steps as for the real voltage supply, we will just do it a little bit faster by using this time Kirchhoff's current law in one point, this point, where we can write that the current i_p going through this branch when we supply an external resistor R_e being passed by a current i_e , which creates a voltage drop U_{Re} on the external resistor, voltage that we will also find between these points and these points. On this knot n here, we can say that i_{cc} is equal to i_p plus i_e .

Notes

Summary



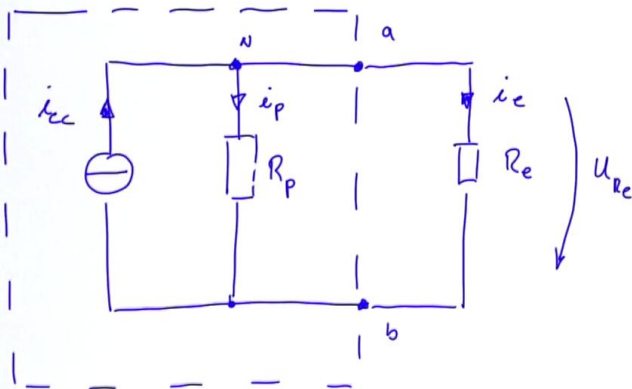

Source de courant réelle

Notion : $i_{cc} = i_p + i_e$; $R_{eq} = \frac{R_e R_p}{R_e + R_p}$ et $U_e = R_{eq} \cdot i_{cc}$; $i_e = \frac{U_e}{R_e}$

- Si $R_e = 0 \rightarrow i_e = i_{cc}$ (courant maximal) "court-circuit"
- Si $R_e = \infty \rightarrow i_e = 0$ et $U_e = R_p \cdot i_{cc}$ (tension maximale) "circuit-ouvert"

Electrotechnique I



We can put the resistors R_p and R_e , in parallel, which gives us a resistance, that we call R_{eq} for equivalent, which is the product of the sum, and which make the voltage at the terminals of the circuit, the voltage U_e , equal to the current i_{cc} that passes through the resistor R_{eq} , which is then equal to R_{eq} multiplied by i_{cc} . We can also write that i_e is equal to U_e over R_e . Once again, to characterise this supply, if we take the extreme cases, namely if the load resistor is equal to zero, we have a current i_e which is equal to the current i_{cc} , we are in the case of a maximal current that the supply can provide, we are once again in short-circuit. The other extreme case, if the external resistor is equal to infinity, well we have an external current equal to zero and a voltage at the terminals of the dipole ab, where U_e which is equal to R_e multiplied by i_{cc} , is also the maximum voltage that can appear at the terminals of the dipole, and we are in the case of an open circuit. Lets graphically represent the characteristic U_i of this supply. Of we represent U_e on the abscissa and i_e on the ordinate, we have a maximum current, equal to i_{cc} , a maximal voltage which is given here and is equal to R_p times i_{cc} , we have the no-load mode and here the short-circuit mode.

Notes

Summary



SOURCE DE COURANT RÉELLE

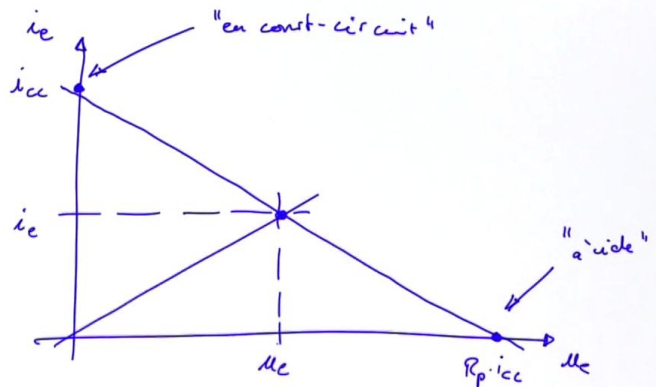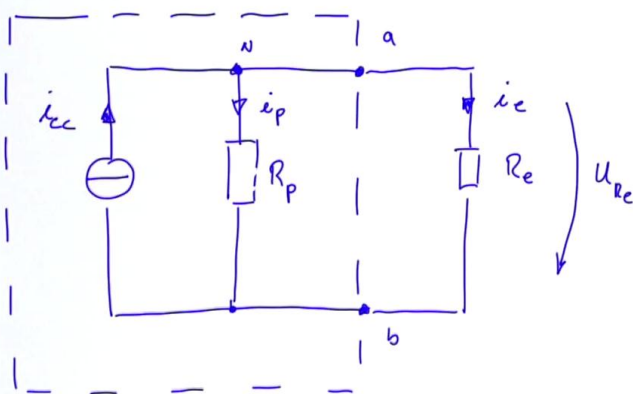

Source de courant réelle

Nœud : $i_{cc} = i_p + i_e$; $R_{eq} = \frac{R_e R_p}{R_e + R_p}$ et $u_e = R_{eq} \cdot i_{cc}$; $i_e = \frac{u_e}{R_e}$

- Si $R_e = 0 \rightarrow i_e = i_{cc}$ (courant maximal) "en court-circuit"
- Si $R_e = \infty \rightarrow i_e = 0$ et $u_e = R_p \cdot i_{cc}$ (tension maximale) "circuit-ouvert"

Electrotechnique I



Once again, everything being linear, we can connect these two points to get the current-voltage characteristic with an intersection point with the external resistor which is given by the intersection of the two curves, the characteristic and the load line, for the operating points u_e and i_e .

Notes

Summary



EQUIVALENCE DES SOURCES DE TENSION ET DE COURANT RÉELLES

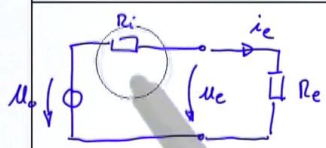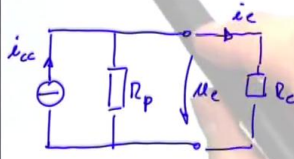Source réelle	Courant de court-circuit ($R_e = 0$)	Tension à vide ($R_e = \infty$)
	$i_{e0} = \frac{U_0}{R_i}$	$U_{e\infty} = U_0$
	$i_{e0} = i_{cc}$	

Electrotechnique I

We will now see what we can do to make these two types of supplies equivalent. I redraw the diagram of the real voltage supply here, with a no-load voltage U_0 , and an internal resistance R_i , a voltage at the terminals of the circuit equal to U_e , and a load R_e which means that a current i_e is passing through the circuit. For the current supply, we have here a current supply equal to i_{cc} , an internal resistor in parallel, which form the supply's dipole, at which appears a voltage at the terminals when we connect an internal resistor R_e and a current i_e passing through. If we look at the short-circuit current in both cases, well the short-circuit current, that we call i_{e0} for the voltage supply, this current i_e is equal to U_0 divided by the internal resistor, when this resistor R_e is equal to zero. In the case of the current supply, when the resistor R_e is equal to zero, well the short-circuit current is equal to i_{cc} , all the current passes through the external resistor. When looking at the no-load voltages, so when the external resistor is infinite, well the no-load voltage that we call infinite U_e , is equal to U_0 in the case of a real voltage supply. Why?



Notes


Summary



25m 00s

EQUIVALENCE DES SOURCES DE TENSION ET DE COURANT RÉELLES

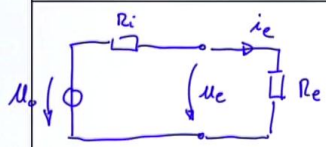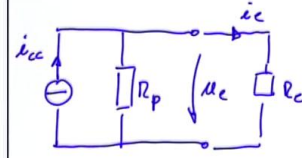Source réelle	Courant de court-circuit ($R_e = 0$)	Tension à vide ($R_e = \infty$)
	$i_{e_0} = \frac{U_0}{R_i}$	$U_{e_\infty} = U_0$
	$i_{e_0} = i_{cc}$	$U_{e_\infty} = R_p \cdot i_{cc}$

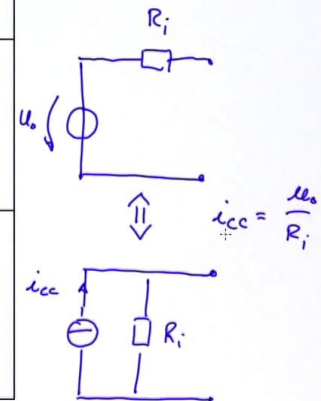

$$\frac{U_0}{R_i} = i_{cc} \quad U_0 = R_p \cdot i_{cc}$$

Equivalence : $R_i = R_p$

Electrotechnique I

Because the current i_e being null, there is no voltage drop at the terminals of R_i and we will find again the voltage U_0 at the terminals of the circuit U_e . In the case of the current supply, the no-load voltage is equal to R_p times i_{cc} , it is the voltage that appears at the circuit terminals when the resistor is infinite, namely when there is no current here, all the current passes through the resistor R_p and so the no-load voltage at the terminals of R_p is equal to i_{cc} times R_p . So for these two supplies to be equivalent, the two short-circuit current must be equal, first condition, so U_0 over R_i must be equal to i_{cc} , second condition, the two no-load voltages must also be equal, so U_0 must be equal to R_p to i_{cc} . In summary, we get the equivalence if R_i is equal to R_p . This means that when we have an ideal voltage supply, with an internal resistor R_i , ideal voltage supply U_0 , that form a real voltage supply, well we can transform in, and conversely, with an ideal current supply of value i_{cc} with an internal resistor R_i by applying the following relation: i_{cc} is equal to U_0 over R_i . Inversely, if we have a real current supply, we can transform it into a real voltage supply by placing a resistor in parallel and a resistance in series and by transforming this current supply in a voltage supply of value R_i times i_{cc} .

Notes

Summary





- Maîtrise d'un circuit complet
- Traitement du circuit
- Analyse
- Autres méthodes

Electrotechnique I

There, after having seen all the simple elements individually, we have the tools to master a complete circuit. We have seen the method to process a circuit and the analysis that are possible to do. Thereafter, we will see new circuit transformation methods.

Notes

Summary



29m 37s