



## Généralités



- Source réelle ( $u_0, R_i$ ) – Charge  $R_L$
- Puissance fournie par la source à la charge
- Valeur maximale de puissance
- Adaptation - Condition
- Rendement
- Conclusion

Electrotechnique I

Hello. Today we will discuss about the power transmitted by a real voltage supply to a load. First of all, we will define the real voltage supply and the load. We will then calculate the power provided by the supply to the load. Then, we will calculate the maximal value of the power as function of the value of the load resistance. We will then define the condition of adaptation. And finally, we will calculate the efficiency of the system and we will end with a conclusion.


Notes

Summary



0m 04s
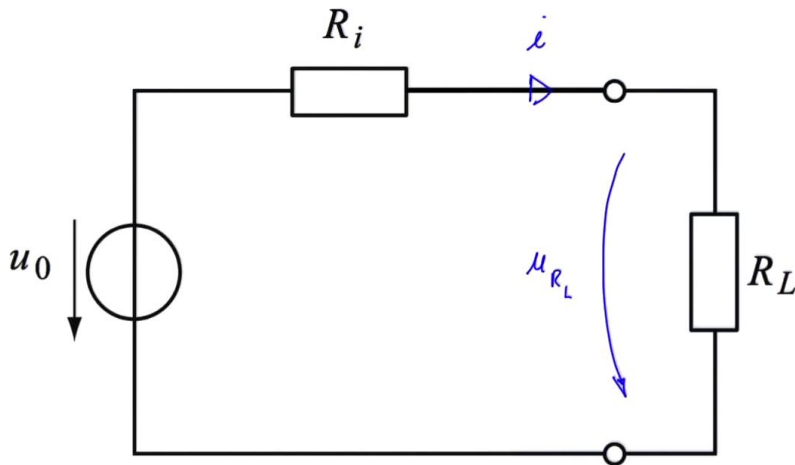
## Source de tension réelle – Charge – Puissance



$$i = \frac{u_0}{R_i + R_L}$$

$$P_{R_L} = u_{R_L} \cdot i = R_L \cdot i^2$$

Electrotechnique I

On this sketch, we see on the left part, the ideal voltage supply and the internal resistance that is both, the real voltage supply and on the right side, the load resistance. On this circuit we can define two values: the current that goes through the circuit, there is just one loop, there is just one current, and the voltage at the terminals of the load resistor that we call  $u_R$  indication L. By Kirchhoff we find very easily, as long as the two resistors are in series, the current that goes through the circuit. We have that  $i$  is equal to  $u_0$  divided by  $R_i + R_L$ . In terms of the power, power that is dissipated in the resistor  $R_L$ , we can write that this power is the product of the voltage drop at the terminals of the resistor multiplied by the current, therefore it is  $u_{R_L}$  multiplied by the current and if we replace the voltage drop at the terminals of the resistor by the resistance times  $i$ ,  $u$  is equal to  $R_L$ , we get that the power is equal to  $R_L$  multiplied by  $i$  squared. By replacing the value of  $i$  by the expression found here above, we finally write that the power in the load resistor is equal to  $(u_0^2 \cdot R_L) / (R_L + R_i)^2$ . This is the first result.


Notes

Summary



0m 36s
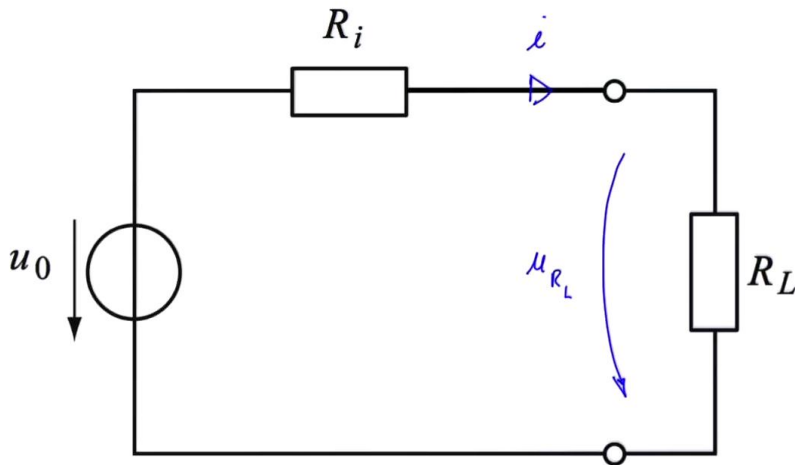
## Source de tension réelle – Charge – Puissance



$$i = \frac{u_0}{R_i + R_L}$$

$$P_{R_L} = u_{R_L} \cdot i = R_L \cdot i^2$$

$$P_{R_L} = \frac{u_0^2 R_L}{(R_L + R_i)^2}$$

$$\text{Si } R_L = 0 \rightarrow P_{R_L} = 0$$

$$\text{Si } R_L = \infty \rightarrow P_{R_L} = \frac{u_0^2 R_L}{R_L^2} = \frac{u_0^2}{R_L} = 0$$

Electrotechnique I

If we analyse this function, we see that in two extreme cases, when the load resistance is zero, then the power in this resistor is also zero. On the other extreme, if the load resistance is infinite, we have a power in this load that is equal to the term  $R_L$  becoming much bigger than  $R_i$  we can express  $R_i$ , we have  $(u_0^2 \cdot R_L) / R_L^2$ , it is equal to  $u_0^2 / R_L$  and it is also equal to zero. Therefore we see that for two extreme values the power is zero. And in between, there is necessarily a maximum, it is this maximum that we will calculate.


Notes

Summary


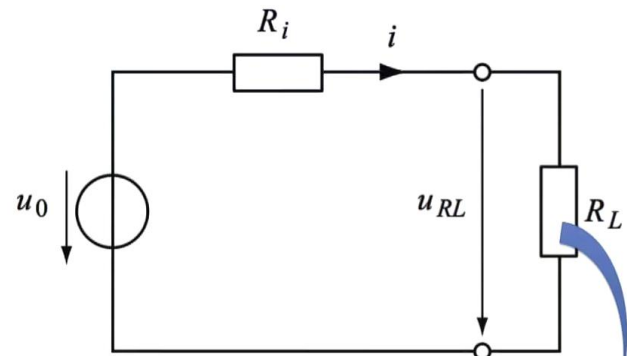
## Puissance maximale

$$\begin{aligned}
 \max \rightarrow \frac{dP}{dR_L} &= 0 & f &= R_L \cdot u_0^2 \\
 & & g &= (R_L + R_i)^2 \\
 & & f' &= u_0^2 \\
 & & g' &= 2(R_L + R_i) \\
 & = \frac{f'g - g'f}{g^2} \\
 \frac{dP}{dR_L} &= \frac{(R_L + R_i)^2 - 2(R_L + R_i)R_L}{(R_L + R_i)^4}
 \end{aligned}$$



$$P_{RL} = \frac{u_0^2 R_L}{(R_L + R_i)^2} = \frac{f}{g}$$

Electrotechnique I

Is repeated on this slide the results obtained earlier. We have represented the same sketch and the power dissipated in the load resistor is given by this equation. To get the maximum of this function with the load resistor  $R_L$  as a variable, we just have to derivate this function with respect to the variable  $R_L$ . Therefore the maximum is found when the derivative of the power with respect to  $R_L$  is equal to zero. To calculate this derivative, we will write that this power function is equal to a numerator that is a function  $f$  divided by the denominator of function  $g$   $f$  is therefore equal to  $R_L \times u_0^2$ , it is the numerator. The denominator  $g$  is equal to  $(R_L + R_i)^2$ . And to calculate this derivative, we know that the derivative is equal to  $(f'g - g'f)/g^2$ . We now calculate the derivative of the function  $f$ , that we call  $f'$ , derivative with respect to  $R_L$  that is equal to  $u_0^2$ , and the derivative of the denominator  $g'$  that is equal to  $2(R_L + R_i)$ . We can therefore replace these functions and those derivatives in this equation and is obtained for the derivative function power with respect to the variable  $R_L$  that it is equal to... the numerator divided by the denominator squared which is equal to  $(R_L + R_i)^{-4}$ .

Notes

Summary



3m 33s

## Puissance maximale


$$\begin{aligned} \max \rightarrow \frac{dP}{dR_L} &= 0 & P &= R_L \cdot u_0^2 \\ & & g &= (R_L + R_i)^2 \\ & & f' &= u_0^2 \\ & & g' &= 2(R_L + R_i) \\ & & &= \frac{f'g - g'f}{g^2} \end{aligned}$$

$$\frac{dP}{dR_L} = \frac{(R_L + R_i)^2 - 2(R_L + R_i)R_L}{(R_L + R_i)^4} = 0$$

$$R_L^2 + 2R_iR_L + R_i^2 - 2R_LR_i - 2R_L^2 = 0$$

$$-R_L^2 + R_i^2 = 0$$

$$\underline{R_L = R_i}$$

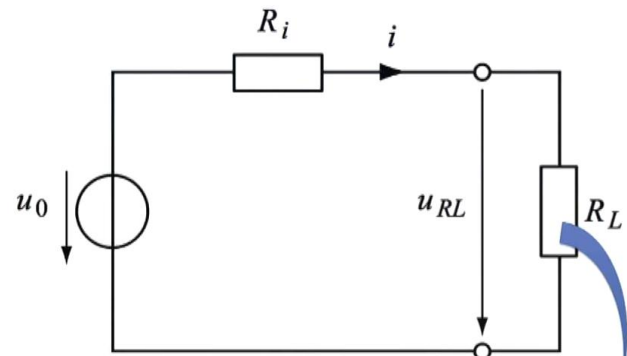

$$P_{RL} = \frac{u_0^2 R_L}{(R_L + R_i)^2} = \frac{P}{g}$$

Electrotechnique I

And we will like to find a zero value of this derivative so we just have to say that the numerator is equal to zero, that we expand and rewrite here... we can simplify it by writing it like  $-R_L^2 + R_i^2 = 0$  and we then find the condition for what we call power adaptation which means that when  $R_L$  is equal to  $R_i$ .

Notes

Summary




5m 55s
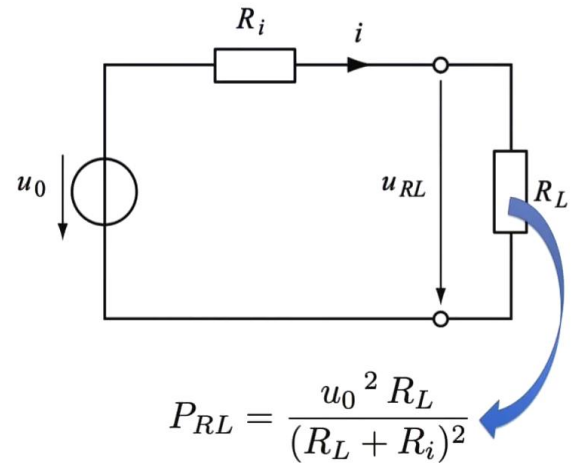
## Puissance maximale

Condition :  $R_L = R_i$

La condition d'adaptation de puissance est donc réalisée lorsque la valeur de la résistance de charge et celle de la résistance interne de la source sont égales



Electrotechnique I

We have now found the power adaptation condition that is fulfilled when the value of the load resistor is equal to the value of the internal resistance. In this case, we say that the load is adapted to the power supply.

Notes

Summary



6m 40s


## Rendement

$$\eta = \frac{P_{\text{utile}}}{P_{\text{fournie source}}} = \frac{R_L \cdot i^2}{(R_L + R_i) \cdot i^2}$$

$$\eta = \frac{R_L}{R_L + R_i}$$

À l'adaptation, donc pour  $R_L = R_i$ , on a :
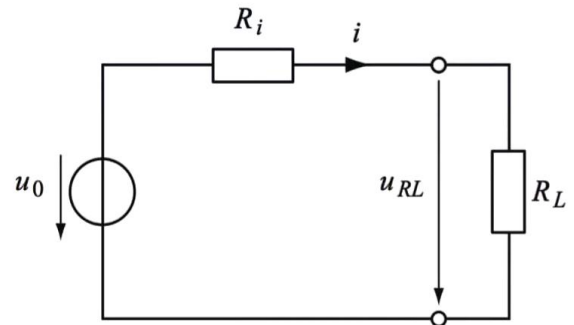
$$\eta_{\text{adaptation}} = \frac{R_L}{2 R_L} = 0.5 \quad \text{pour } P_{\text{max}}$$



Electrotechnique I

Now lets calculate the efficiency of the system. The efficiency is determined by the ratio between the useful power, which means the power given to the load resistor, it is here represented by this little green arrow here, divided by the total power given by the power supply. This total power given by the power supply is represented here by the big green arrow. Therefore the useful power in the load resistor is  $R_L \times i^2$ . And the total power given by the power supply is the current squared times the sum of two resistors, which is  $(R_L + R_i) \times i^2$ . We can rewrite this formula in a simpler way. So the efficiency is given by the load resistance divided by the sum of the two resistors, load resistor and internal resistance. Let's look what is happening concerning the adaptation efficiency, so when the load resistance is equal to the internal resistance. We have the adaptation efficiency that is equal to  $R_L / (R_L + R_i)$  but these two values being equal, we simply have that the efficiency is equal to  $R_L / 2 R_L$  if we replace  $R_i$  by  $R_L$  which are equal, so we have a 50% efficiency for  $P_{\text{max}}$  and therefore 50% for the adaptation.



Notes

Summary




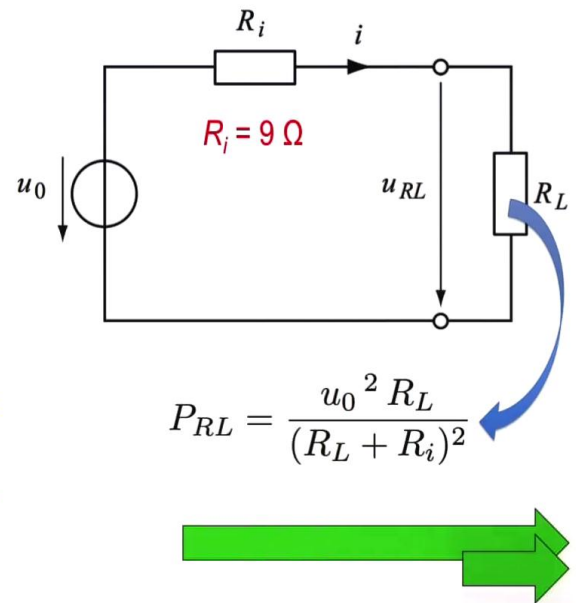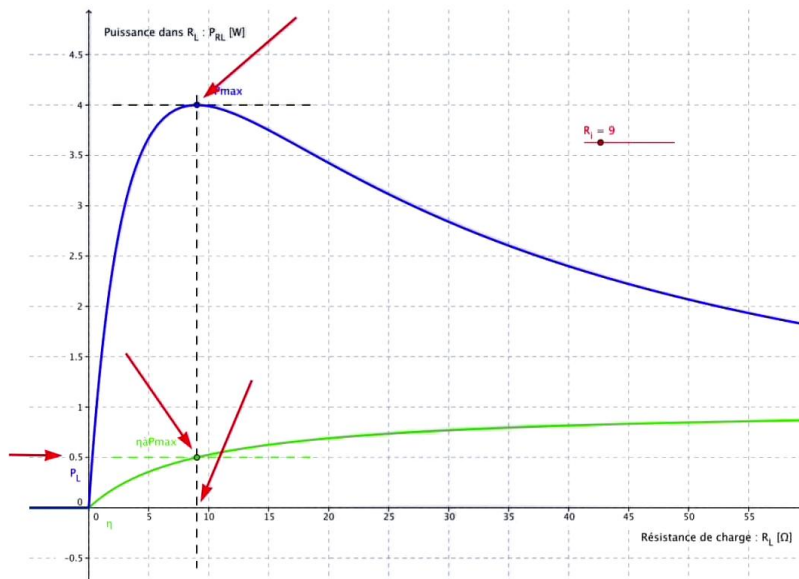
## Courbe de puissance maximale $P_{RL} = f(R_L)$



$$P_{RL} = \frac{u_0^2 R_L}{(R_L + R_i)^2}$$



Electrotechnique I



Let's take an example with numerical values. We recover here our real voltage supply with the load resistance, let's take the case of an internal resistance that is equal to 9 ohms. We can calculate the power as function of  $R_L$ . We have traced it here, it is the blue curve. We see that the maximum power, here, is for a value  $R_L$ , 9 ohms. We also see that for this load resistor value, the adaptation efficiency is 0.5 therefore 50%. So on this graph, we can see that the maximum power that can be transmitted to the load resistance  $R_L$  is not only depending on  $R_L$  but it is also very dependent on the internal resistance. We can see that there is a limit to the power given by the voltage supply. If we take another value with a higher internal resistance, therefore a less performant real voltage supply, we see that the maximal power decreases by this equation, but most of all the maximum is now again at a value that is equal to the value of the load resistance that matches the value of the internal resistance, so 12.5 ohms, and again the efficiency at this value is 50%.

Notes

Summary


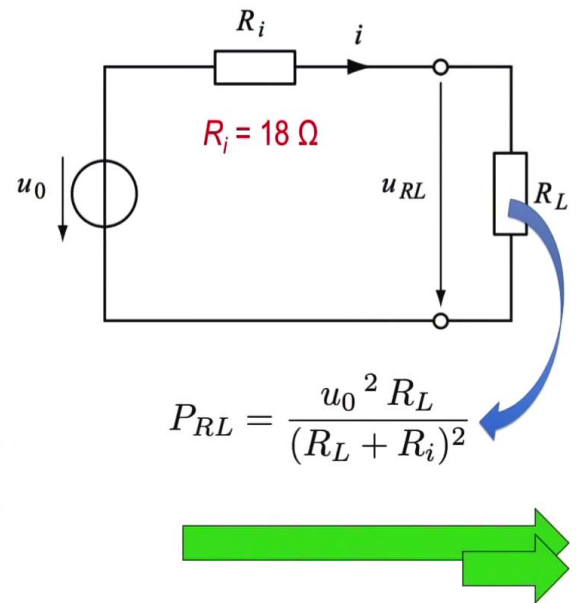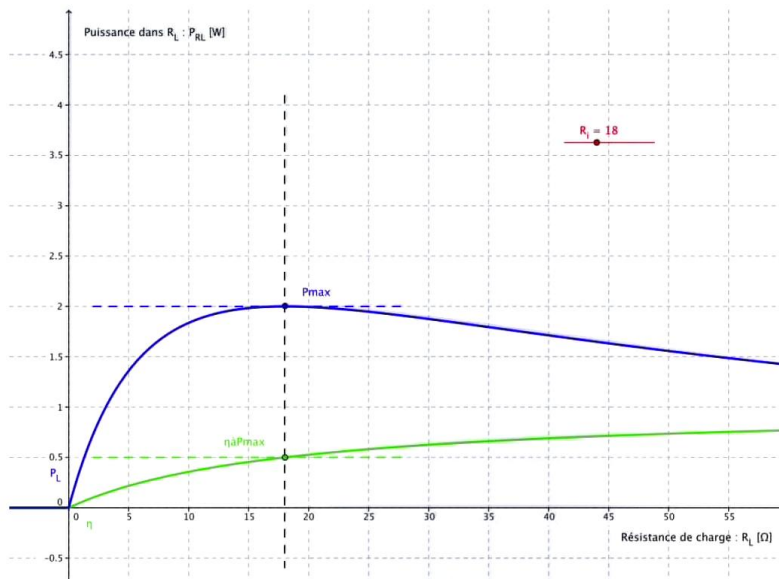
## Courbe de puissance maximale $P_{RL} = f(R_L)$



Electrotechnique I

If we take a third internal resistance therefore a real voltage supply of lower quality with a higher internal resistance, the maximum power is again smaller but we recover the same adaptation conditions for the load resistor at the value of the internal resistance and the efficiency is 50% at the value of the internal resistance. If we consider a battery to power a car for example, electric, this battery can be modelled with a first approach by this real voltage supply with a no-load voltage and an internal resistance that represents the chemistry of the battery, the connectivity, the electrodes... worse the battery is lower the power thus bigger the internal resistance is and less power can be transmitted to the load therefore to the electric motor. We mostly see that we can not transmit an infinite power but a power that depends on the internal resistance.

Notes

Summary



10m 54s



- Une source réelle et sa charge sont adaptées l'une à l'autre si  $R_i$  et  $R_L$  sont égales
- A l'adaptation :
  - la puissance transmise par la source à la charge est maximale
  - le rendement est alors de 50 %

Electrotechnique I

In conclusion, we can say two things. First, a real voltage supply and its load are adapted in power to one another if the internal resistance of the real supply voltage is equal to the load resistance. And secondly, The power transmitted by the supply to the load is maximum and secondly, the adaptation efficiency is 50%. We understand it well because there is as much power that is dissipated in the internal resistance then in the load resistance because they are equal Thank you for your attention.

Notes

Summary



12m 05s