

Généralités



- Rappel
 - Puissance active P et réactive Q
 - Puissance apparente S
 - Somme de puissances
- Exercice
- Conclusion

Electrotechnique I

Hello, welcome to this new lesson of the Electrotechnics course. Today, we will solve an exercise by the powers method using only partially the complex calculation to determine the impedances, currents and voltages. We will begin with a very brief recall of the notions acquired on the powers and their additivity rules. We will then see a concrete example.

Notes

Summary




0m 04s

Puissances active, réactive et apparente - Rappel

$$P_{tot} = \sum_j P_j$$

$$Q_{tot} = \sum_j Q_j$$
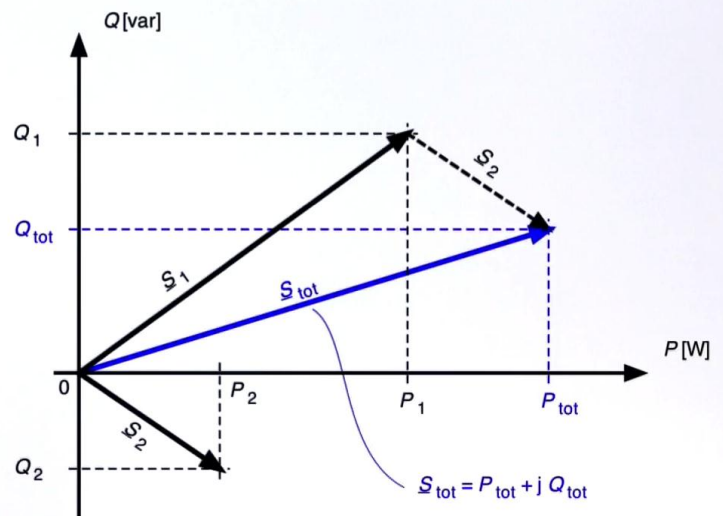
$$\underline{S}_{tot} = \sum_j \underline{S}_j = P_{tot} + jQ_{tot}$$



Electrotechnique I


So, as a reminder, the active power P is represented on the real axis of the complex plane and the reactive power Q on the imaginary axis of the same complex plane. The additive rule for a system of several elements says that: the total active power is the sum of powers for each system. same for the total reactive power: it is the algebraic sum of the reactive power units. We can perform this addition algebraically, why? Because these variables are collinear. In this example, we see that we have two systems: the system S_1 and the system S_2 , and each of them consumes an active power, P_1 and P_2 , that we will be able to add; and a reactive power Q_1 and Q_2 . Here, pay attention, Q_2 is negative, and we can also add the reactive powers. Concerning the apparent power, we can also add them, but it is vector addition. We see here that the total apparent power, is the sum of the apparent power S_1 plus the apparent power S_2 , vector. And then, we can find the total power, the total active power, as the sum of P_1 and P_2 : We see that it corresponds to the real part of the complex apparent power, it is that term here. Same for the total reactive power, it is the sum of Q_1 and of Q_2 , Q_2 being negative, and it corresponds to the imaginary part of the complex apparent power.

Notes

Summary



Résolution par les puissances - Exemple

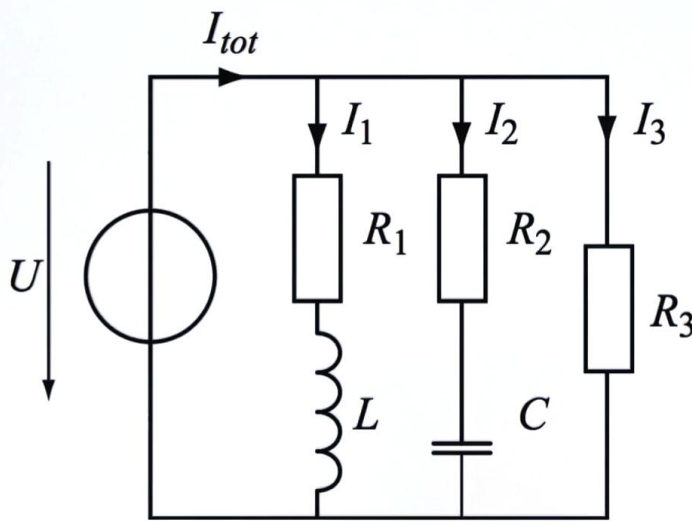

On demande de calculer :

- la puissance active totale
- la puissance réactive totale
- la puissance apparente totale
- le courant débité par la source
- le facteur de puissance total

Electrotechnique I


Let's now see a concrete example. We have the following circuit that is composed of an excitation, an alternative voltage U that will feed three branches of a circuit: a branch RL , a branch RC , and a third branch that is only made of a resistor. And in each of these branches, a current will flow I_1 , I_2 and I_3 , and we ask to compute the total active power of all the circuit, the total reactive power as well, and the total apparent power, and last, we ask the total current delivered by the supply. Finally, we ask also, the total power factor, that is to say, the power factor seen by this supply U .

Notes

Summary



Résolution par les puissances - Exemple

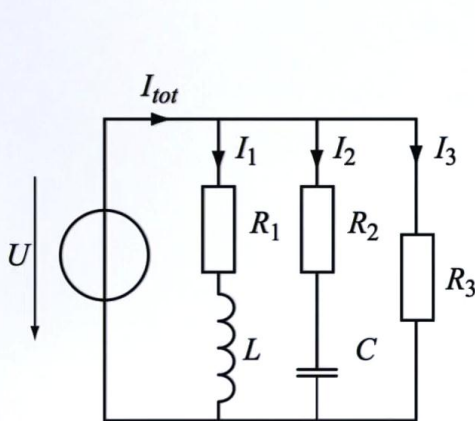

Branche 1 : $Z_1 = \sqrt{R_1^2 + (\omega L)^2}$
 $I_1 = U / Z_1$

Branche 2 : $Z_2 = \sqrt{R_2^2 + \left(\frac{1}{\omega C}\right)^2}$
 $I_2 = U / Z_2$

Branche 3 : $I_3 = \frac{U}{R_3}$

Electrotechnique I


In order to solve that exercise, we will compute the three currents I_1 , I_2 , I_3 in each branch and we will compute the norm of the current; why? Because, to determine the active power, we only need to know : I ; to square it, multiply it by R to get that active power. same for the reactive power that is equal to x multiplied by I^2 . To determine the current, we still need to know the impedance Z_1 , this impedance Z_1 is given by: Pythagoras R_1^2 plus x_1 , namely, ωL squared. This, is the value of the norm of the impedance. The norm of the current will then be equal to U divided by Z_1 . Same for the branch n°2. The impedance's norm, Z_2 is equal to the square root of the real part squared namely, R_2^2 of the impedance Z_2 plus the imaginary part it's then a capacitor it's $1/\omega C$ squared. And then, the norm of the current I_2 is given by U/Z_2 . Finally, for the third branch, it is simpler because we have only one resistive part, we have the current I_3 given by U / Z_3 or R_3 . The imaginary part is null. Therefore, we can now compute all the active and reactive powers for each of the three branches.

Notes

Summary



Résolution par les puissances - Exemple

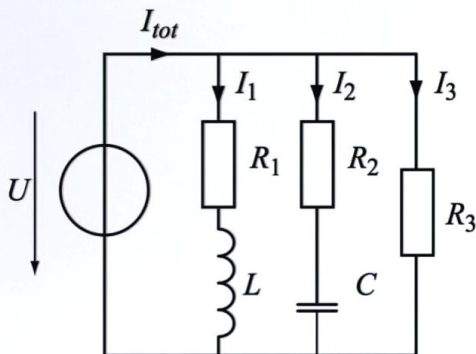

Branche 1 : $Z_1 = \sqrt{R_1^2 + (\omega L)^2}$
 $I_1 = U/Z_1$

$$\begin{cases} P_1 = R_1 \cdot I_1^2 = \frac{U^2 \cdot R_1}{R_1^2 + \omega^2 L^2} \\ Q_1 = \omega L \cdot I_1^2 = \frac{U^2 \cdot \omega L}{R_1^2 + \omega^2 L^2} \end{cases}$$

Branche 2 : $Z_2 = \sqrt{R_2^2 + \left(\frac{1}{\omega C}\right)^2}$
 $I_2 = U/Z_2$

$$\begin{cases} P_2 = R_2 \cdot I_2^2 = \frac{U^2 \cdot R_2}{R_2^2 + 1/\omega^2 C^2} \\ Q_2 = -\frac{I_2^2}{\omega C} = \frac{-U^2 / \omega C}{R_2^2 + 1/\omega^2 C^2} \end{cases}$$

Branche 3 : $I_3 = \frac{U}{R_3}$

$$\begin{cases} P_3 = R_3 \cdot I_3^2 = U^2 / R_3 \\ Q_3 = 0 \end{cases}$$

Electrotechnique I


We have that P_1 , is equal to R_1 times I_1^2 , which is equal to R_1 times the current squared, that is to say, we will develop this term, U^2 divided by Z squared then it is R_1^2 plus $\omega^2 L^2$, times the resistance R_1 . For the reactive power in this branch, it is always equal to, x_1 times I_1^2 , then, x it's ωL multiplied by I_1^2 . And it is equal, after development, to the current I_1 , U^2 over Z squared, times x_1 , namely ωL . For the active power in the second branch, we have that P_2 is equal to R_2 times I_2^2 , the norm of I_2 squared, and is equal to I^2 , namely U^2 divided by Z^2 , that is to say; $R^2 + 1 / \omega^2 C^2$, times R_2 . For the reactive power, it is x the reactive part of the branch, namely, negative. minus one over ωC times I_2^2 . And this is equal to $-U^2 / \omega C$ divided by the norm squared, of Z_2 , namely $R_2^2 + 1/\omega^2 C^2$. Finally, for the third branch, the active power is equal to R_3 times I_3^2 , it is equal to U^2/R_3 . And the reactive part is equal to zero, because there is no reactance in this branch.

Notes

Summary



Résolution par les puissances - Exemple

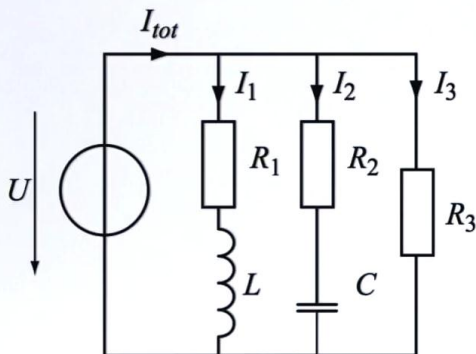

Puissance active totale :

$$P_{tot} = \sum_{j=1}^3 P_j = \frac{U^2 R_1}{R_1^2 + \omega^2 L^2} + \frac{U^2 R_2}{R_2^2 + 1/\omega^2 C^2} + \frac{U^2}{R_3}$$

Puissance réactive totale :

$$Q_{tot} = \sum_{j=1}^3 Q_j = \frac{U^2 \omega L}{R_1^2 + \omega^2 L^2} - \frac{U^2 / \omega C}{R_2^2 + 1/\omega^2 C^2}$$

Puissance apparente totale, courant total et facteur de puissance :

$$S_{tot} = \sqrt{P_{tot}^2 + Q_{tot}^2} \quad ; \quad I_{tot} = \frac{S_{tot}}{U} \quad ; \quad \cos \varphi = \frac{P_{tot}}{S_{tot}}$$

Electrotechnique I

The total active power consumed by the circuit is given by the relation that the total power is the sum of all the active powers, and it is equal to : [Writes on the blackboard] This is the result. For the total reactive power, we can also sum all the reactive powers of the circuit, and it is equal to : [Writes on the blackboard] Here is the result for the total reactive power. Now, it is very simple by Pythagoras, to extract the apparent power from the circuit. It is given by the square root of $P_{tot}^2 + Q_{tot}^2$. This result allows us to determine very easily the norm of the total current knowing that the apparent power is U times I , therefore, the current I_{tot} is equal to the total apparent power divided by U . We see at that level that we have managed to determine the norm of the total current without performing the vector sum of three unit currents. and, we arrive at the last question of the exercise. We have to calculate the global $\cos \varphi$ of the circuit. And it is given, we have seen it before, by the total active power divided by the total apparent power. We could determine the value of $\cos \varphi$ by computing the equivalent impedance of the five impedances, and we would found the same result, the same $\cos \varphi$, but probably the calculation is longer.

Notes

Summary





- Calcul de toutes les puissances dans le circuit
 - P_j , Q_j et S_j
- La méthode permet d'éviter les calculs complexes explicites
 - Le calcul de la norme des courants est suffisante

$$P = R \cdot I^2 \quad \text{et} \quad Q = X \cdot I^2$$
 - La phase des courants n'est pas nécessaire

Electrotechnique I

That's it, we have computed all the powers in the circuit: - The active power P which is the algebraic sum of all the active powers of the elements. - The reactive power Q which is also the algebraic sum of all the reactive powers of all the elements. - And the apparent power S which is, this time, the vector sum of all the apparent powers in the circuit. The method avoids the explicit complex calculations, only the norm of the currents is sufficient; Why? Because the powers are calculated only with the norm of the current with the active power, it's RI^2 ; the reactive power it's x times I^2 . The phase of the currents and the impedances, it is not necessary to calculate it. Thank you for your attention.

Notes

Summary



10m 37s