



- Introduction
- Charge non équilibrée
- Cas d'une charge en triangle
- Cas d'une charge en étoile
- Conclusion

Electrotechnique II

Hello, welcome to the 7th lesson, dedicated to non-symmetrical three-phase systems. In this lesson, we will define what a non-symmetrical three-phase charge is and we will see how, by connecting it in a wye or delta setup on a grid we will be able to calculate the current or the voltage in each of the charge's branches, letting us define the different values of a three-phase grid, such as the active power, the reactive power or the apparent power.


Notes

Summary



0m 00s
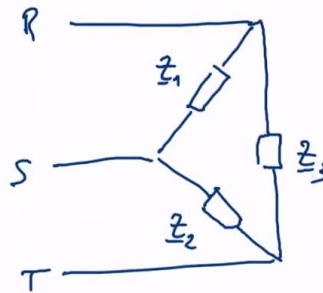
$$\underline{Z}_1 \neq \underline{Z}_2 \neq \underline{Z}_3$$



The non-balanced charge, or non-symmetrical, is easy to define: it is actually a three-phase charge whose three impedances are not strictly identical. We will then have \underline{Z}_1 different than maybe \underline{Z}_2 which is different than \underline{Z}_3 in a setup for example, in which, in delta, we have the three impedances, here with R, S and T, \underline{Z}_1 , \underline{Z}_2 and \underline{Z}_3 . When can this happen ? This can firstly happen with a defect in a machine, a machine or a charge on which one of the impedances has been voluntarily changed or either a default, for example, when one of the charges has a defective connection and one of the impedances is suddenly disconnected. This implies that \underline{Z}_2 and \underline{Z}_3 should be identical, \underline{Z}_1 is then disconnected and switches to 0. We then face the case of a non-symmetrical charge or non-balanced charge.


Notes

Summary



CAS D'UNE CHARGE EN TRIANGLE
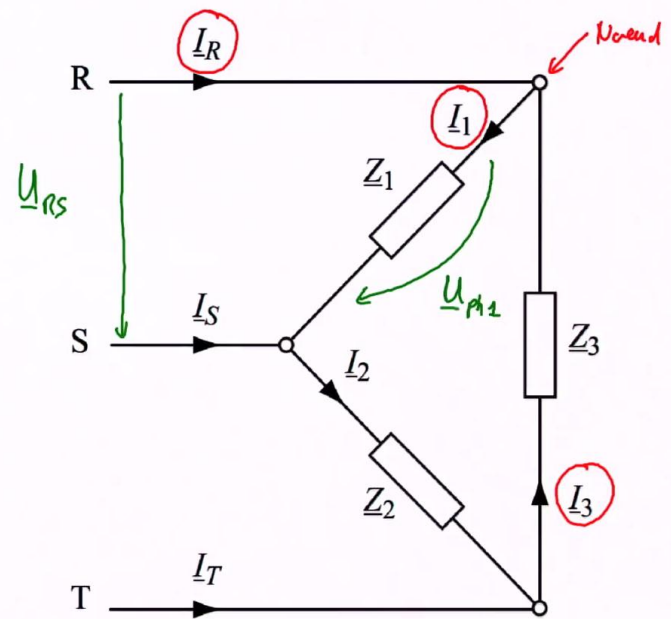
$$\underline{U}_{RS} = \sqrt{3} U e^{j\frac{\pi}{6}}$$



Electrotechnique II

The first study case will be that of this non-symmetrical charge that will be connected using a delta setup. We will see that it is the easiest study that we can make, which can seem paradoxical, but we will see that this way of connecting in delta is actually quite easy to resolve, even for a non-symmetrical case. We remind the elementary values that we have seen previously, that is to say we have here the line voltage, the \underline{U}_{rs} which will be equal to this phase voltage so I will write it \underline{U}_{ph1} . However, as we have seen when studying the delta mode, the line current \underline{I}_R will be equal, by Kirchhoff, to the subtraction between \underline{I}_1 and \underline{I}_3 since we have this knot here. So the Kirchhoff equations will greatly help us to resolve such a problem of a non-symmetrical charge since, finally, knowing that Z_1 , Z_2 and Z_3 are different, we just need to apply, in a relatively simple way, Kirchhoff. Then, we remind you what the three line voltage \underline{U}_{rs} , \underline{U}_{st} and \underline{U}_{tr} are equal to in a symmetrical grid. Thus, \underline{U}_{rs} is equal to $\sqrt{3} \cdot U \cdot e^{j(\pi/6)}$. We then have a shift of 120 degrees for \underline{U}_{st} with $\sqrt{3} \cdot U \cdot e^{j(-\pi/2)}$ and the third \underline{U}_{tr} $\sqrt{3} \cdot U \cdot e^{j(5\pi/6)}$.


Notes

Summary



CAS D'UNE CHARGE EN TRIANGLE

$$\begin{aligned}\underline{U}_{RS} &= \sqrt{3} U e^{j \frac{\pi}{6}} \\ \underline{U}_{ST} &= \sqrt{3} U e^{j (-\frac{\pi}{2})} \\ \underline{U}_{TR} &= \sqrt{3} U e^{j \frac{5\pi}{6}} \\ \underline{I}_1 &= \frac{\underline{U}_{ph1}}{\underline{Z}_1} = \frac{\underline{U}_{RS}}{\underline{Z}_1} \\ \underline{I}_2 &= \frac{\underline{U}_{ST}}{\underline{Z}_2} \\ \underline{I}_3 &= \frac{\underline{U}_{TR}}{\underline{Z}_3}\end{aligned}$$

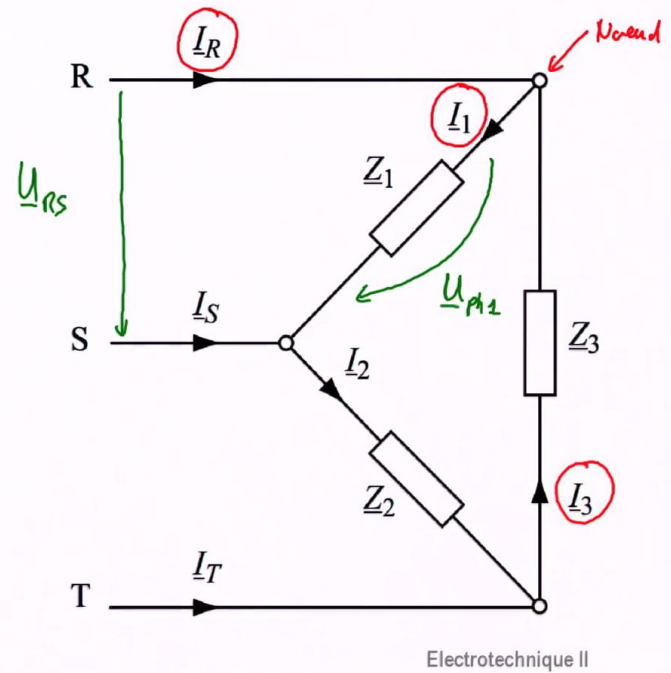

Electrotechnique II

This being said, and knowing that the phase voltage on the terminals of each impedance Z is equal to the line voltage, we can calculate, each time, for the three values, this time in an individual manner, since we have a non-symmetrical system, we can calculate \underline{I}_1 which is equal to the phase voltage \underline{U}_{ph1} divided by \underline{Z}_1 but this phase voltage \underline{U}_{ph1} , as shown on the drawing, is also \underline{U}_{RS} divided by \underline{Z}_1 . This gives me the phase current \underline{I}_1 and in the same way, will be able to calculate \underline{I}_2 : \underline{U}_{ST} divided by \underline{Z}_2 , and \underline{I}_3 : \underline{U}_{TR} divided by \underline{Z}_3 . Now that we have \underline{I}_1 , \underline{I}_2 , \underline{I}_3 , we can, on each knot, calculate the line currents \underline{I}_R , \underline{I}_S and \underline{I}_T .

Notes

Summary



CAS D'UNE CHARGE EN TRIANGLE

$$\underline{I}_R = \underline{I}_1 - \underline{I}_3$$

$$\underline{I}_S = \underline{I}_2 - \underline{I}_1$$

$$\underline{I}_T = \underline{I}_3 - \underline{I}_2$$

Electrotechnique II

The three line current are calculated by applying once again Kirchhoff on the knot, as shown previously and then \underline{I}_R is equal to \underline{I}_1 minus \underline{I}_3 . I remind you that it is a vectorial subtraction. \underline{I}_S is equal to \underline{I}_2 minus \underline{I}_1 and \underline{I}_T is equal to \underline{I}_3 minus \underline{I}_2 . The calculations are then quite long, but relatively simple and need the calculation for each branch considered separately, since it is non-symmetrical. It is evident that, in a symmetrical case, we only look at one branche and all the other branches are simply shifted by 120 degrees. It is not the case here and each branch must be calculated individually.

Notes

Summary



5m 10s


CAS D'UNE CHARGE EN ÉTOILE

2 possibilités :

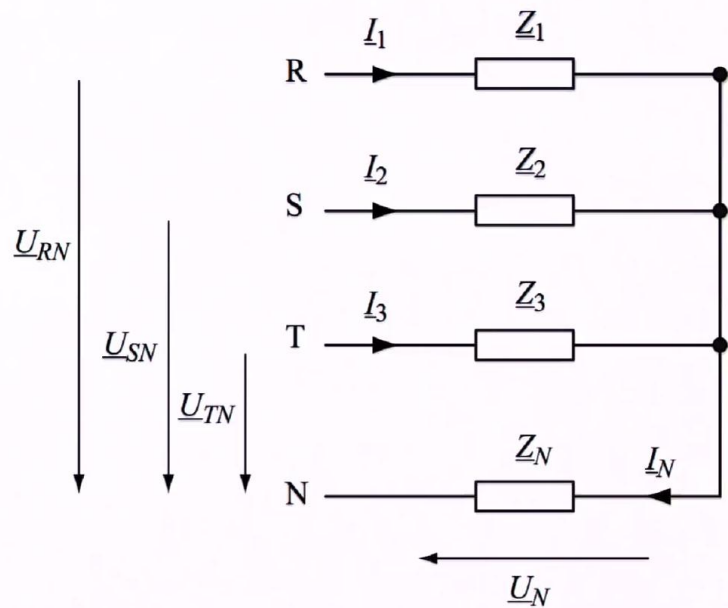a) Neutre non connecté :

→ $\gamma \rightarrow \Delta$

→ appliqué la technique
précédente : Kirchhoff



Electrotechnique II

Now in the case of a charge which is, this time, connected with a wye setup. In a wye setup, you have here the presented diagram, with shows a non-symmetrical impedance connected in a wye manner, with classically, a neutral point that appears and that be connected or not to the network's neutral. Thus, we will have two cases, two solutions, if you want to starting off with this diagram here and we need to define now which of these cases we are handling. So two possibilities. The first is that we have this wye charge whose neutral is not connected. Often, the neural is not connected to the network, so it is possible to have a case like ours if the neutral is not connected. This will be our case a) non-connected neutral, so the easiest way to resolve such a problem is to take the circuit that is in a wye setup, and convert the charge as for a delta setup. When it is for a delta setup, we can apply the previous technique, namely the application of Kirchhoff's rules on the circuit, this time, a delta system. Then, the conversion from wye to delta is done as seen in the previous lessons using the rules for the calculations of the impedances Z_1 , Z_2 and Z_3 which pass in a wye setup, or a delta setup.

Notes

Summary




CAS D'UNE CHARGE EN ÉTOILE

2 possibilités :

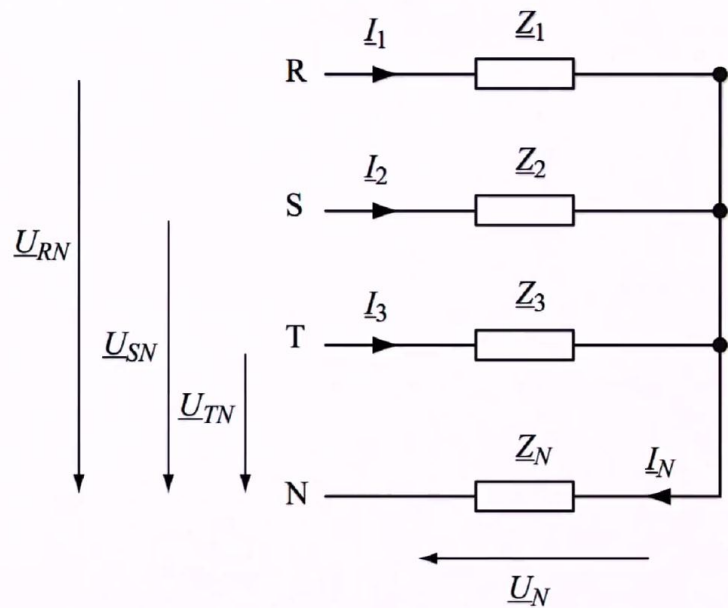a) Neutre non connecté :

→ $\gamma \rightarrow \Delta$

→ appliquer la technique
précédente : Kirchhoff



Electrotechnique II

That is the easiest. Once we have a non-connected neutral, it is enough to convert this circuit or this charge for a wye setup, and to pass it in a delta setup, before applying Kirchhoff's technique.

Notes

Summary



8m 02s

CAS D'UNE CHARGE EN ÉTOILE

b) Neutre est connecté :

$$\underline{I}_R = \frac{\underline{U}_{RN} - \underline{U}_N}{\underline{Z}_1}$$

$$\underline{I}_S = \frac{\underline{U}_{SN} - \underline{U}_N}{\underline{Z}_2}$$

$$\underline{I}_T = \frac{\underline{U}_{TN} - \underline{U}_N}{\underline{Z}_3}$$

$$\underline{I}_N = \frac{\underline{U}_N}{\underline{Z}_N}$$

$$\rightarrow \underline{I}_N = \underline{I}_R + \underline{I}_S + \underline{I}_T$$

Electrotechnique II

In the second case b), where the neutral is connected. Here things obviously change as we have an impedance Z_n , which is the impedance through which the neutral current will pass, to go back to the source, that needs to be taken into account. We then need to calculate a certain number of values that will depend on the neutral voltage. In particular, we have a line current that can be calculated, still using Kirchhoff, by taking the U_{rn} minus U_n and this divided by the impedance Z_1 . We can say, in the same way, for I_s U_{sn} minus U_n divided by Z_2 , and finally the third current in the branche t, or in the line t, is U_{tn} so the phase voltage, minus U_n divided by Z_3 . We can also say that the neutral current, in the neutral which is normally zero in a symmetrical charge, but which will be non zero in the non-symmetrical case it is then equal to this voltage U_n divided by the impedance coming back from the neutral Z_n . We can also say that, and we know it, this neutral current, by Kirchhoff, is the sum of the three line current, that meet up. From there, we can then replace a certain number of elements that come from what we indicated previously, namely $I_n = I_r + I_s + I_t$ and so, we replace with the three elements that we have calculated here I_r , I_s and I_t .

Notes

Summary



CAS D'UNE CHARGE EN ÉTOILE

b) Newton est commutée :

$$\underline{I}_R = \frac{\underline{U}_{RN} - \underline{U}_N}{\underline{Z}_1}$$

$$\underline{I}_S = \frac{\underline{U}_{SN} - \underline{U}_N}{\underline{Z}_2}$$

$$\underline{I}_T = \frac{\underline{U}_{TN} - \underline{U}_N}{\underline{Z}_3}$$

$$\underline{I}_N = \frac{\underline{U}_N}{\underline{Z}_N}$$

$$\rightarrow \underline{I}_N = \underline{I}_R + \underline{I}_S + \underline{I}_T$$

$$\underline{I}_N = \frac{\underline{U}_{RN}}{\underline{Z}_1} + \frac{\underline{U}_{SN}}{\underline{Z}_2} + \frac{\underline{U}_{TN}}{\underline{Z}_3} - \underline{U}_N \left[\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3} \right]$$

$$\underline{U}_N = \left[\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3} + \frac{1}{\underline{Z}_N} \right]^{-1} \left[\frac{\underline{U}_{RN}}{\underline{Z}_1} + \frac{\underline{U}_{SN}}{\underline{Z}_2} + \frac{\underline{U}_{TN}}{\underline{Z}_3} \right]$$

Electrotechnique II

What does this give us? This gives us the following equation. \underline{I}_N I put on one side the phase voltages and on the other the neutral voltages, so we have \underline{U}_{RN} divided by \underline{Z}_1 plus \underline{U}_{SN} divided by \underline{Z}_2 plus \underline{U}_{TN} divided by \underline{Z}_3 minus and we have the neutral voltage that come here, evidently, and that multiplies 1 divided by \underline{Z}_1 plus 1 divided by \underline{Z}_2 plus 1 divided by \underline{Z}_3 . This is equal to, I repeat it, the neutral voltage divided by \underline{Z}_N . We will then eliminate the current \underline{I}_N in this equation and make the top equation, here and the bottom equation equal. In this way, we eliminate the neutral current and we can set down the equation by writing \underline{U}_N equal and then, by extracting the neutral voltage. We find \underline{U}_N equal firstly to 1 divided by \underline{Z}_1 , plus 1 divided by \underline{Z}_2 plus 1 divided by \underline{Z}_3 plus 1 divided by \underline{Z}_N and all this at the power -1 that multiplies \underline{U}_{RN} divided by \underline{Z}_1 plus \underline{U}_{SN} divided by \underline{Z}_2 , plus \underline{U}_{TN} divided by \underline{Z}_3 . To be clearer, I eliminate what I put here to get the whole equation and then what do we still need to do? The whole work is now to calculate \underline{U}_{RN} by taking, each time, the voltage \underline{U}_{rs} that we have here and by subtracting this voltage \underline{U}_N of the neutral that we have just calculated, of course in a vectorial way.

Notes

Summary



b) Newton est connecté :

$$\underline{I}_R = \frac{\underline{U}_{RN} - \underline{U}_N}{\underline{Z}_1}$$

$$\underline{I}_S = \frac{\underline{U}_{SN} - \underline{U}_N}{\underline{Z}_2}$$

$$\underline{I}_T = \frac{\underline{U}_{TN} - \underline{U}_N}{\underline{Z}_3}$$

$$\underline{I}_N = \frac{\underline{U}_N}{\underline{Z}_N}$$

$$\rightarrow \underline{I}_N = \underline{I}_R + \underline{I}_S + \underline{I}_T$$

$$\underline{I}_N = \frac{\underline{U}_{RN}}{\underline{Z}_1} + \frac{\underline{U}_{SN}}{\underline{Z}_2} + \frac{\underline{U}_{TN}}{\underline{Z}_3} - \underline{U}_N \left[\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3} \right]$$

$$\underline{U}_N = \left[\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3} + \frac{1}{\underline{Z}_N} \right]^{-1} \left[\frac{\underline{U}_{RN}}{\underline{Z}_1} + \frac{\underline{U}_{SN}}{\underline{Z}_2} + \frac{\underline{U}_{TN}}{\underline{Z}_3} \right]$$

Electrotechnique II

But this lets us calculate the voltage \underline{U}_N , so on the neutral impedance, to determine completely the different values of a non-symmetrical charge that was connected in wye, and whose neutral is connected.

Notes

Summary





- En triangle la charge asymétrique se calcule en utilisant Kirchhoff
- En étoile, si le neutre n'est pas connecté, on passe en triangle puis Kirchhoff. Si le neutre est connecté, on doit calculer la tension U_N

Electrotechnique II

In conclusion, we saw the non-symmetrical charge, we saw how, in a delta setup, we can in a relatively simple way determine these different values and by applying the Kirchhoff equations for the wye setup two cases presented themselves, either the neutral is connected and then we need to calculate everything, in particular the neutral voltage and to a relatively complex vectorial calculation on each of these values. Or else, the neutral is not connected and it is enough to switch from a wye to a delta setup and to repeat what we have seen for the delta setup.

Notes

Summary



12m 56s